

1. Calculate the total resistance in ohms

@ Series

$$R_s = 20 + 30 + 50 \\ = 100 \Omega$$

@ parallel,

$$\frac{1}{R_p} = \frac{1}{20} + \frac{1}{100} + \frac{1}{50} \\ = \frac{1}{0.08} \\ = 12.5 \Omega$$

2. Calculate the total current from power supply

Series

$$I = \frac{V}{R} \\ = \frac{125}{100} \\ = 1.25 \text{ A}$$

~~parallel~~

parallel

$$I = \frac{125}{12.5} \\ = 10 \text{ A}$$

3. Calculate current through each resistor.

Series = 1.25 A

parallel

$$R_1 = \frac{125}{20}$$

$$= 6.25 \text{ A}$$

$$R_2 = \frac{125}{100}$$

$$= 1.25 \text{ A}$$

$$R_3 = \frac{125}{50}$$

$$= 2.5 \text{ A}$$

(4)

Calculate voltage drop through each resistor

Series

$$V = 1.25 \times 20$$

$$= 20 \text{ V}$$

$$V = 1.25 \times 30$$

$$= 37.5 \text{ V}$$

$$V = 1.25 \times 50$$

$$= 62.5 \text{ V}$$

parallel

$$V = 125 \text{ V}$$

5. Calculate the power dissipated through each resistor.

$$\text{Power} = \text{Voltage} \times \text{Current} = VI$$

Series

$$P = VI$$

$$P = 25 \times 1.25 \\ = 31.25 \text{ W}$$

$$P = 37.5 \times 1.25 \\ = 46.875 \text{ W}$$

$$P = 62.5 \times 1.25 \\ = 78.125 \text{ W}$$

parallel

$$P = VI$$

$$P = 125 \times 6.25 \\ = 781.25 \text{ W}$$

$$P = 125 \times 1.25 \\ = 156.25 \text{ W}$$

$$P = 125 \times 2.5 \\ = 312.5 \text{ W}$$